

# Application Note

## Propagation Delay Considerations

AN-CM-283

### Abstract

*This application note illustrates the concept of propagation delay and how to estimate the propagation delay of different circuit blocks. It includes techniques that foster a more robust design implementation.*

---

---

**Propagation Delay Considerations**

**Contents**

**Abstract** ..... 1

**Contents** ..... 2

**Figures**..... 2

**Terms and Definitions**..... 2

**1 References** ..... 2

**2 Introduction**..... 3

**3 Propagation Delay Considerations in GreenPAK** ..... 3

    3.1 Estimating Propagation Delay for Different Blocks ..... 4

**4 Conclusions** ..... 7

**Revision History** ..... 8

**Figures**

Figure 1: Opening Datasheet via Help Window ..... 3

Figure 2: Typical Delay Estimated for Macrocells in SLG46826 ..... 4

Figure 3: Example for Signal Delay ..... 5

Figure 4: Serial Block Propagation Delay..... 5

Figure 5: Design Example ..... 5

Figure 6: Design Example Simulation Result ..... 6

Figure 7: Filtering Glitches Dependent on Propagation Delay (Using P DLY (FILTER))..... 6

Figure 8: Filtering Glitches Dependent on Propagation Delay (Using LUT Buffer)..... 6

**Terms and Definitions**

Tpd	Propagation Delay
LUT	Look-Up Table
P DLY	Programmable Delay

**1 References**

- [1] SLG46826, Datasheet, Dialog Semiconductor.
- [2] AN-1046, Various Edge Detector Circuits, Application Note, Dialog Semiconductor.

Author: Oleh Sapiha

## Propagation Delay Considerations

### 2 Introduction

In digital electronics, the time needed to transmit a signal from one point (element) to another is called propagation delay (Tpd). The main factors that determine additional propagation delay of a signal through an integrated circuit are diode and transistor capacitances between the components of the ICs and inertia of the switching process in diode and transistors. This problem is exacerbated in synchronous systems, where the propagation of a signal through the IC is dependent upon the global clock frequency.

In practice, propagation delay is variable and depends on different factors including environment (for temperature) and electrical characteristics (for example supply voltage). GreenPAK, just like any other IC, has propagation delay resulting from its internal components like LUTs, DFFs, and others.

### 3 Propagation Delay Considerations in GreenPAK

The question of whether propagation delay is advantageous or detrimental is heavily dependent upon the specific circuit. On one hand, the signal delay caused by LUT propagation gives us the possibility to create helpful designs such as edge detectors in reset functions (see application note AN-1046), signal filters, or high frequency oscillators.

On the other hand, propagation can lead to undesirable and unpredictable logic combinations (often called “signal race”), which can negatively influence design functionality. Furthermore, Tpd limits the maximum frequency with which circuits can function. There are a lot of devices and applications that work on a minimum allowable switching frequency, like transmission protocols (I<sup>2</sup>C, UART, SPI), Levels Shifters, and more. Depending upon the minimum propagation delay, certain applications may not be feasible.

We are going to consider this issue and give simple hints that can help to calculate propagation delay of different blocks and their combinational delay. We will also show problems that can be caused by propagation delay, along with the methods to avoid these problems.

To start, we must know where propagation delay timings can be found. To find a typical estimated propagation time for different blocks go to the datasheet. It is very easy to do it via GreenPAK designer. Choose the necessary IC (let's say SLG46826). GreenPAK Designer automatically downloads the datasheet after clicking «Datasheet» in the «Help» window (see [Figure 1](#)).

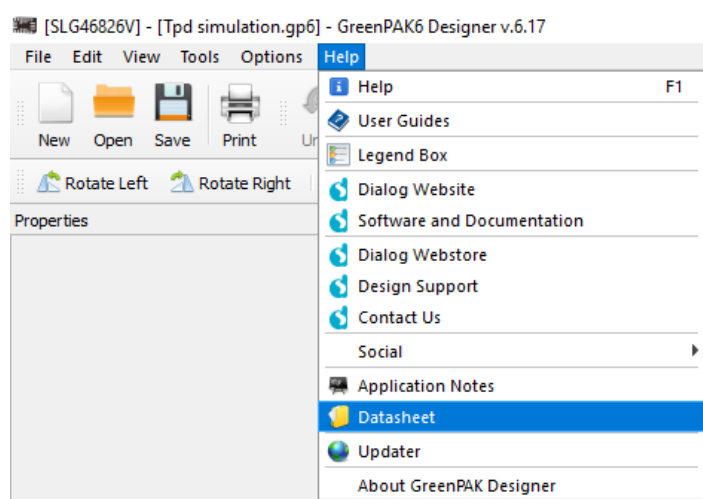


Figure 1 Opening Datasheet via Help Window

## Propagation Delay Considerations

In the datasheet navigate to chapter 3.4 Timing Characteristics of propagation delay can be determined in Table 8 Typical Delay Estimated for Each Macrocell (**Note1:** Chapter and table number example is for the SLG46826 IC, it varies from chip to chip). Looking through the table, the datasheet of a certain block specifies the propagation delay variation for different voltage ranges at 25 °C (**Note 2:** All data shown are worst case and includes 6-sigma coverage factor).

### 3.4 TIMING CHARACTERISTICS

Table 8: Typical Delay Estimated for Each Macrocell at T = 25°C

Parameter	Description	Note	V <sub>DD</sub> = 2.5 V		V <sub>DD</sub> = 3.3 V		V <sub>DD</sub> = 5 V		Unit
			Rising	Falling	Rising	Falling	Rising	Falling	
tpd	Delay	Multi-Function DFF Q	23	21	16	15	11	11	ns
tpd	Delay	Multi-Function DFF nQ	23	21	17	15	12	11	ns
tpd	Delay	Multi-Function DFF nRESET Q	--	29	--	21	--	15	ns
tpd	Delay	Multi-Function DFF nRESET nQ	31	--	22	--	16	--	ns
tpd	Delay	2-bit LUT	17	16	12	12	8	8	ns
tpd	Delay	3-bit LUT	17	17	12	12	8	9	ns
tpd	Delay	4-bit LUT	--	--	--	--	--	--	ns
tpd	Delay	Digital input to Low Voltage to PP 1X	35	222	24	150	16	96	ns
tpd	Delay	Digital input to with Schmitt Trigger to PP 1x	26	30	19	22	13	16	ns
tpd	Delay	Digital input to 1xPP	27	31	19	22	13	16	ns
tpd	Delay	Digital input to 2xPP	24	29	18	21	12	15	ns
tpd	Delay	Digital input to 1xNMOS	--	27	--	20	--	14	ns
tpd	Delay	Digital input to 2xNMOS	--	26	--	19	--	14	ns
tpd	Delay	Digital input to 1x3-State (Z to 0)	--	24	--	17	--	12	ns

Figure 2: Typical Delay Estimated for Macrocells in SLG46826

### 3.1 Estimating Propagation Delay for Different Blocks

Frequently, questions are asked: “what is the maximum frequency that GreenPAK can work with?” or “how do I estimate the delay of an input signal?”. To answer these questions, refer to the following Example 1 and Example 2.

#### Example 1

The datasheet of a certain block specifies that for 2-bit LUT (SLG46826), at the V<sub>DD</sub> = 3.3 V rising edge delay, t<sub>pd</sub> (rising) = 12 ns, falling edge delay t<sub>pd</sub> (falling) = 12 ns. What is the maximum frequency that can go through the LUT?

$$t_{\min} = t_{pd}(\text{rising}) + t_{pd}(\text{falling}) = 12 \text{ ns} + 12 \text{ ns} = 24 \text{ ns}$$

$$f_{\max} = \frac{1}{t_{\min}} = \frac{1}{24 \text{ ns}} = \frac{1}{24 \times 10^{-9}} = 41.66 \times 10^6 \text{ Hz} = 41.66 \text{ MHz}$$

As a result, the received frequency  $f_{\max} = 41.66 \text{ MHz}$  is the highest frequency that can pass through the 2 bit-LUT.

#### Example 2

Given: Logic circuit in [Figure 3](#). Find: signal delay at the output pin (V<sub>DD</sub> = 5 V).

## Propagation Delay Considerations

 


Figure 3: Example for Signal Delay

The solution includes two parts: rising edge delay and falling edge delay calculation.

$$t_{\text{rising\_edge}} = t_{\text{pd}}(\text{rising\_DI\_to\_1xPP}) + t_{\text{pd}}(\text{rising\_2bitLUT}) + 2t_{\text{pd}}(\text{rising\_3bitLUT}) = 13 \text{ ns} + 8 \text{ ns} + 2 \cdot 8 \text{ ns} = 37 \text{ ns}$$

$$t_{\text{falling\_edge}} = t_{\text{pd}}(\text{falling\_DI\_to\_1xPP}) + t_{\text{pd}}(\text{falling\_2bitLUT}) + 2t_{\text{pd}}(\text{falling\_3bitLUT}) = 16 \text{ ns} + 8 \text{ ns} + 2 \cdot 9 \text{ ns} = 42 \text{ ns}$$

 


Figure 4: Serial Block Propagation Delay

Result: rising and falling edges of applied input signal are delayed 37 ns and 42 ns accordingly.

To fully understand potential issues related to Tpd, let's consider the simple logic circuit designed in SLG46826 (Figure 5). A signal that is applied to Input2 goes through an XOR block. The signal is fed into the XOR through IN0 directly, and with IN1 it passes via an AND-cell (Input1 is enable signal).

 


Figure 5: Design Example

So, how will propagation delay factor into this delay? When Input1 is Low, the XOR-gate works to buffer the Input2 signal. But, when it is High, XOR's IN1 will be applied with the signal from Input2, which will be delayed by AND cell propagation delay. This construction generates a short duration glitch on Output2 (Figure 6). Not good, especially for edge-dependent logic on the output.

## Propagation Delay Considerations



Figure 6: Design Example Simulation Result

The first and the easiest way to overcome glitches caused by this circuit scenario is to filter it using either P DLY block (configured as both edge delay) or FILTER (configured as filter) (see Figure 7). This method is reliable because of long delay time (up 834 ns for 4 cells P DLY, according to the datasheet). However, these specialized blocks may already be used for other functions or the input frequency is too high to use P DLY, so another method for filtering propagation glitches should be applied.

The second method is based upon providing the equivalent signal delay for the 2 XOR inputs. In order to implement this, a 2-bit LUT (2-bit LUT is an example, any other block can be used) is added between Input2 and the XOR's In0 (see Figure 8). The extra block equalizes the delays on XOR's inputs, which prevents that logic from creating short glitches on Output2 pin. **Note 3:** Because of the internal structure of LUT's, their inputs have different propagation delay times. The higher the input label number, the shorter the propagation delay it has. For example, IN1 has shorter propagation delay time than IN0.

 


Figure 7: Filtering Glitches Dependent on Propagation Delay (Using P DLY (FILTER))

 


Figure 8: Filtering Glitches Dependent on Propagation Delay (Using LUT Buffer)

---

**Propagation Delay Considerations****4 Conclusions**

In this article, we considered the sensitivity of  $T_{pd}$ , and how to calculate total propagation delay time in GreenPAK designer. Two examples with maximum frequency and signal delay calculation were presented. Two different methods of filtering glitches caused by propagation delay were shown.

---

**Propagation Delay Considerations**

**Revision History**

<b>Revision</b>	<b>Date</b>	<b>Description</b>
1.0	13-Jun-2019	Initial version



## Propagation Delay Considerations

### Status Definitions

Status	Definition
DRAFT	The content of this document is under review and subject to formal approval, which may result in modifications or additions.
APPROVED or unmarked	The content of this document has been approved for publication.

### Disclaimer

Unless otherwise agreed in writing, the Dialog Semiconductor products (and any associated software) referred to in this document are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of a Dialog Semiconductor product (or associated software) can reasonably be expected to result in personal injury, death or severe property or environmental damage. Dialog Semiconductor and its suppliers accept no liability for inclusion and/or use of Dialog Semiconductor products (and any associated software) in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Information in this document is believed to be accurate and reliable. However, Dialog Semiconductor does not give any representations or warranties, express or implied, as to the accuracy or completeness of such information. Dialog Semiconductor furthermore takes no responsibility whatsoever for the content in this document if provided by any information source outside of Dialog Semiconductor.

Dialog Semiconductor reserves the right to change without notice the information published in this document, including, without limitation, the specification and the design of the related semiconductor products, software and applications. Notwithstanding the foregoing, for any automotive grade version of the device, Dialog Semiconductor reserves the right to change the information published in this document, including, without limitation, the specification and the design of the related semiconductor products, software and applications, in accordance with its standard automotive change notification process.

Applications, software, and semiconductor products described in this document are for illustrative purposes only. Dialog Semiconductor makes no representation or warranty that such applications, software and semiconductor products will be suitable for the specified use without further testing or modification. Unless otherwise agreed in writing, such testing or modification is the sole responsibility of the customer and Dialog Semiconductor excludes all liability in this respect.

Nothing in this document may be construed as a license for customer to use the Dialog Semiconductor products, software and applications referred to in this document. Such license must be separately sought by customer with Dialog Semiconductor.

All use of Dialog Semiconductor products, software and applications referred to in this document is subject to Dialog Semiconductor's [Standard Terms and Conditions of Sale](http://www.dialog-semiconductor.com), available on the company website ([www.dialog-semiconductor.com](http://www.dialog-semiconductor.com)) unless otherwise stated.

Dialog, Dialog Semiconductor and the Dialog logo are trademarks of Dialog Semiconductor Plc or its subsidiaries. All other product or service names and marks are the property of their respective owners.

© 2019 Dialog Semiconductor. All rights reserved.

## Contacting Dialog Semiconductor

### United Kingdom (Headquarters)

*Dialog Semiconductor (UK) LTD*  
Phone: +44 1793 757700

### Germany

*Dialog Semiconductor GmbH*  
Phone: +49 7021 805-0

### The Netherlands

*Dialog Semiconductor B.V.*  
Phone: +31 73 640 8822

### Email:

[enquiry@diasemi.com](mailto:enquiry@diasemi.com)

### North America

*Dialog Semiconductor Inc.*  
Phone: +1 408 845 8500

### Japan

*Dialog Semiconductor K. K.*  
Phone: +81 3 5769 5100

### Taiwan

*Dialog Semiconductor Taiwan*  
Phone: +886 281 786 222

### Web site:

[www.dialog-semiconductor.com](http://www.dialog-semiconductor.com)

### Hong Kong

*Dialog Semiconductor Hong Kong*  
Phone: +852 2607 4271

### Korea

*Dialog Semiconductor Korea*  
Phone: +82 2 3469 8200

### China (Shenzhen)

*Dialog Semiconductor China*  
Phone: +86 755 2981 3669

### China (Shanghai)

*Dialog Semiconductor China*  
Phone: +86 21 5424 9058